

# Hardware Verification

## Specification and Verification with Higher-Order Logic

Arnd Poetzsch-Heffter  
(Slides by Jens Brandt)

Software Technology Group  
Fachbereich Informatik  
Technische Universität Kaiserslautern


Sommersemester 2008

# Outline

- 1 Introduction
- 2 Hardware Verification in HOL
  - General Approach
  - Composition
  - Verification
  - Full Adder Example
- 3 Summary

# Why Formal Hardware Verification?

## Example (Simple Sampler)

 

## Informal Specification

The input line **datain** accepts a stream of bits, and the output line **dataout** emits the same stream delayed by four cycles. The bus **out** is four bits wide. If the input **sample** is false then the 4-bit word at **out** is the last four bits input at **datain**. Otherwise, the output word is all zeros.

# Inadequacies of Informal Specification

## Problems

- The informal specification is vague:
  - Does ‘the last four bits input’ include the current bit?
- The informal specification is incomplete:
  - What is the value at **dataout** during the first three cycles?
- The informal specification is unusable:
  - Natural language can't easily be simulated or compiled!

# Outline

## 1 Introduction

## 2 Hardware Verification in HOL


- General Approach
- Composition
- Verification
- Full Adder Example

## 3 Summary

# Formal Specification in HOL

## General Approach

Consider the following device **Dev**

 

specified by a boolean term **Dev**(*a*, *b*, *c*, *d*)

$$\text{Dev}(a, b, c, d) = \begin{cases} T & \text{if } a, b, c, \text{ and } d \text{ could occur} \\ & \text{simultaneously on the corresponding} \\ & \text{external wires of the device Dev} \\ F & \text{otherwise} \end{cases}$$

# Combinational Specification Examples


## Example (Exclusive-or (XOR) Gate)



$$\vdash \text{Xor}(i_1, i_2, o) = (o = \neg(i_1 = i_2))$$

$$\mathbf{Xor} : \text{bool} \times \text{bool} \times \text{bool} \rightarrow \text{bool}$$

## Example (Bidirectional Wires)

 

$$\vdash \text{Ntran}(g, s, d) = (g \Rightarrow (d = s))$$

$$\mathbf{Ntran} : \text{bool} \times \text{bool} \times \text{bool} \rightarrow \text{bool}$$


# Sequential (Time-Dependent) Devices

## Example (Unit delay)

$$\vdash \text{Del}(in, out) = \forall t. out(t+1) = in\ t$$

$$\text{Del} : (time \rightarrow bool) \times (time \rightarrow bool) \rightarrow bool$$
 
## Example (Rising edge triggered DTYPE register)



$$\vdash \text{Dtype}(ck, d, q) = \forall t. q(t+1) = \text{if Rise } ck\ t \text{ then } d\ t \text{ else } q\ t$$

$$\vdash \text{Rise } ck\ t = \neg ck(t) \wedge ck(t+1)$$

$$\text{Dtype} : (time \rightarrow bool) \times (time \rightarrow bool) \times (time \rightarrow bool) \rightarrow bool$$



# Specification of the Sampler

## Example (Sampler)

- Identify *time* with 'number of clock cycles' so  $time = nat$
- We can specify the sampler formally by

$$\forall t :: nat. (dataout(t) = datain(t-4)) \wedge$$

$$(out(t) = \text{if } sample(t)$$

$$\text{ then } [F; F; F; F] \text{ else } [datain(t-4);$$

$$datain(t-3);$$

$$datain(t-2);$$

$$datain(t-1)])$$

# Formal Specification



The formal specification is

- **precise**  
'the last four bits input' does not include the current bit.
- **complete**  
can infer that  $dataout$  equals  $datain(0)$  during the first three cycles  
(assuming  $m < n \Rightarrow (m - n = 0)$ )
- **usable**  
the predicate calculus notation can be processed by machine


...but you need some knowledge to read it

# Composing Behaviours

Consider the following two devices

  
 $\mathcal{S}_1[a, x]$  $\mathcal{S}_2[x, b]$ 

Conjunction ( $\wedge$ ) models connecting components together

 
 $\mathcal{S}_1[a, x] \wedge \mathcal{S}_2[x, b]$

# Hiding Internal Structure

Consider the composite device

 

 Existential quantification ( $\exists$ ) 'hides' internal wires



# Why does it work?

## Hiding Internal Behaviour

- $D_1 f_1 (a, x) = (x = f_1 a)$
- $D_2 f_2 (x, b) = (b = f_2 x)$

$$\begin{aligned}
 & D(f_1, f_2)(a, b) \\
 = & \exists x. D_1 f_1 (a, x) \wedge D_2 f_2 (x, b) \\
 = & \exists x. (x = f_1 a) \wedge (b = f_2 x) && \text{expanding definitions} \\
 = & \exists x. (x = f_1 a) \wedge (b = f_2(f_1 a)) && \text{unwinding} \\
 = & (\exists x. (x = f_1 a)) \wedge (b = f_2(f_1 a)) && \text{narrowing scope of } \exists \\
 = & \top \wedge (b = f_2(f_1 a)) && \text{properties of } \exists \\
 = & (b = f_2(f_1 a)) && \text{property of } \wedge
 \end{aligned}$$

# In HOL

## Example (Composition in HOL)

```
consts f1 :: "(bool => bool)"
```

```
consts f2 :: "(bool => bool)"
```

```
fun DevIO :: "(bool => bool) => (bool * bool) => bool" where  
  "DevIO f (x,y) = (y = f x)"
```

```
constdefs D1 :: "(bool * bool) => bool"  
  "D1 == DevIO f1"
```


```
constdefs D2 :: "(bool * bool) => bool"  
  "D2 == DevIO f2"
```

```
fun D :: "(bool * bool) => bool" where  
  "D (a,b) = (EX x. D1 (a,x) & D2 (x,b))"
```

```
lemma "D (a,b) = (b = f2 (f1 a))"
```


# Another example

## Example (Composed System)

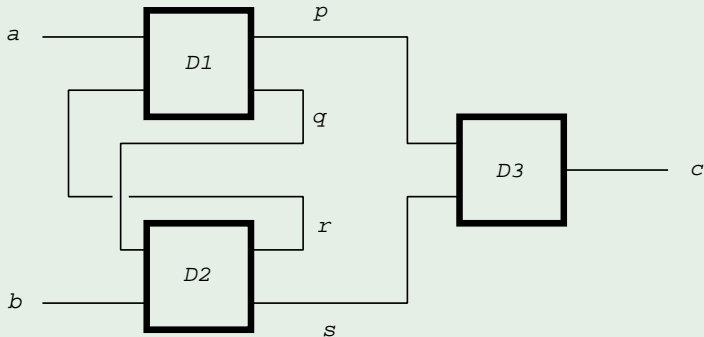

# Another example

## Example (Composed System)

 

```
consts f1, f3, f4, f5 :: "(bool * bool) => bool"
```

```
consts f2 :: "bool => bool"
```

```
fun D1 :: "(bool * bool * bool * bool) => bool" where
```

```
"D1 (w,x,y,z) = ( y = f1 (w,x) & z = f2 w )"
```

```
fun D2 :: "(bool * bool * bool * bool) => bool" where
```

```
"D2 (w,x,y,z) = ( y = f3 (w,x) & z = f4 (w,x) )"
```

```
fun D3 :: "(bool * bool * bool) => bool" where
```

```
"D3 (x,y,z) = ( z = f5 (x,y) )"
```

```
fun D :: "(bool * bool * bool) => bool" where
```

```
"D (a,b,c) = (EX p q r s. D1 (a,r,p,q) & D2 (q,b,r,s) & D3 (p,s,c) )"
```

```
lemma "D (a,b,c) = (c = f5 (f1 (a,(f3 ((f2 a),b))), (f4 ((f2 a),b))))"
```




# Formulating Correctness

## What means correct?

- The strongest formulation is **equivalence**  
 $\vdash \forall v_1 \dots v_n. \mathcal{M}[v_1, \dots, v_n] = \mathcal{S}[v_1, \dots, v_n]$
- For *partial* specifications, use **implication**  
 $\vdash \forall v_1 \dots v_n. \vdash \mathcal{M}[v_1, \dots, v_n] \Rightarrow \mathcal{S}[v_1, \dots, v_n]$
- In general, the satisfaction relationship in  
 $\vdash \mathcal{M}[v_1, \dots, v_n]$  satisfies  $\mathcal{S}[v_1, \dots, v_n]$   
must be one of **abstraction**.

# A Simple Correctness Proof

## Example (CMOS Inverter)

 

Suppose we wish to verify that  $o = \neg i$ .

## Three Steps

- define a model of the circuit in logic
- formulate the correctness of the circuit
- prove the correctness of the circuit

# Formal specifications of CMOS Primitives

## Simple switch model

$$\begin{array}{c} g \\ | \\ s \text{---} \text{---} \text{---} d \end{array} \vdash \text{Ptran}(g, s, d) = (\neg g \Rightarrow (d = s))$$


$$\begin{array}{c} g \\ | \\ s \text{---} \text{---} \text{---} d \end{array} \vdash \text{Ntran}(g, s, d) = (g \Rightarrow (d = s))$$

$$\begin{array}{c} g \\ | \\ \perp \\ \equiv \end{array} \vdash \text{Gnd } g = (g = F)$$

$$\begin{array}{c} \circ \\ | \\ p \end{array} \vdash \text{Pwr } p = (p = T)$$

# Design Model and Correctness

## Example (CMOS Inverter)

 

- The design is modelled using composition and hiding:  
 $\vdash \text{Inv}(i, o) = \exists g p. \text{Pwr } p \wedge \text{Gnd } g \wedge \text{Ntran}(i, g, o) \wedge \text{Ptran}(i, p, o)$
- Correctness is formulated by the equivalence:  
 $\vdash \forall i o. \text{Inv}(i, o) = (o = \neg i)$

# The Correctness Proof

## Example (CMOS Inverter)

- Definition of Inv:

$$\vdash \text{Inv}(i, o) = \exists g p. \text{Pwr } p \wedge \text{Gnd } g \wedge \text{Ntran}(i, g, o) \wedge \text{Ptran}(i, p, o)$$

- Expanding with definitions:

$$\vdash \text{Inv}(i, o) = \exists g p. (p = \text{T}) \wedge (g = \text{F}) \wedge \\ (i \Rightarrow (o = g)) \wedge (\neg i \Rightarrow (o = p))$$

- By simple logical reasoning:

$$\vdash \text{Inv}(i, o) = (i \Rightarrow (o = \text{F})) \wedge (\neg i \Rightarrow (o = \text{T}))$$

- Simplifying gives:

$$\vdash \text{Inv}(i, o) = (i \Rightarrow \neg o) \wedge (\neg i \Rightarrow o)$$

# The Correctness Proof

## Example (CMOS Inverter)

$$\vdash \text{Inv}(i, o) = (i \Rightarrow \neg o) \wedge (\neg i \Rightarrow o)$$

- By the law of the contrapositive:  
$$\vdash \text{Inv}(i, o) = (o \Rightarrow \neg i) \wedge (\neg i \Rightarrow o)$$
- By the definition of boolean equality:  
$$\vdash \text{Inv}(i, o) = (o = \neg i)$$
- Generalizing the free variables gives:  
$$\vdash \forall i o. \text{Inv}(i, o) = (o = \neg i)$$

# In HOL

## Example (CMOS Inverter)

```
fun Pwr :: "bool => bool" where "Pwr p = (p = True)"
```

```
fun Gnd :: "bool => bool" where "Gnd p = (p = False)"
```

```
fun Ntran :: "(bool * bool * bool) => bool" where "Ntran (x,y,z) = (x --> y=z)"
```

```
fun Ptran :: "(bool * bool * bool) => bool" where "Ptran (x,y,z) = (~x --> y=z)"
```

```
fun Inv :: "(bool * bool) => bool" where
```

```
  "Inv (inp,out) = (EX p g. Pwr p & Gnd g & Ntran (inp,g,out) & Ptran(inp,p,out))"
```

```
lemma "Inv (inp,out) = (out = (~inp))"
```

# Hardware Verification in HOL


## Scope of the Method

- The inverter example is, of course, trivial!
- But the same method has been applied to
  - a commercial CMOS cell library,
  - several (small) complete microprocessors
  - complex signed-binary arithmetic hardware
  - many other systems, large and small
- Features of the approach:
  - the specification language is just logic
    - logic can mimic HDL constructs
  - the rules of reasoning are also pure logic
    - special-purpose derived rules are possible
  - big formal proofs require machine assistance



# Bigger example

## Example (Full Adder)

 

## In HOL

## Example (Full Adder)

```
fun Add1 :: "(bool * bool * bool * bool * bool) => bool" where
```

```
"Add1(a,b,cin,sum,cout) =
```

```
(EX p0 p1 p2 p3 p4 p5 p6 p7 p8 p9 p10 p11.
```

```
  Ptran(p1,p0,p2) & Ptran(cin,p0,p3) & Ptran(b,p2,p3) & Ptran(a,p2,p4) &
  Ptran(p1,p3,p4) & Ntran(a,p4,p5) & Ntran(p1,p4,p6) & Ntran(b,p5,p6) &
  Ntran(p1,p5,p11) & Ntran(cin,p6,p11) & Ptran(a,p0,p7) & Ptran(b,p0,p7) &
  Ptran(a,p0,p8) & Ptran(cin,p7,p1) & Ptran(b,p8,p1) & Ntran(cin,p1,p9) &
  Ntran(b,p1,p10) & Ntran(a,p9,p11) & Ntran(b,p9,p11) & Ntran(a,p10,p11) &
  Pwr(p0) & Ptran(p4,p0,sum) & Ntran(p4,sum,p11) & Gnd(p11) &
  Ptran(p1,p0,cout) & Ntran(p1,cout,p11) )"
```


```
constdefs Bv :: "bool => nat"
```

```
"Bv x == if x then 1 else 0"
```

```
lemma "Add1(a,b,cin,sum,cout) = (2*(Bv cout) + Bv sum = Bv a + Bv b + Bv cin)"
```

# Ripple-Carry Adder
 
## Example (An $n$ -bit ripple-carry adder)



We wish to prove that:

- $(2^n \times cout) + s = a + b + cin$
- (note that  $cout, s, a, b, cin$  are numbers)
- There are, as usual, three steps ...

# Notation for Bits and Words

## Bits and Words

- Bits are represented by booleans
  - T represents 1 and F represents 0
- $Bv\ b$  is the number represented by  $b$ 
  - $Bv : bool \rightarrow nat$
  - $Bv\ b = \text{if } b \text{ then } 1 \text{ else } 0$
- Words are represented as lists of booleans
  - the head of a list represents the most significant bit
  - example: 1011 represented as  $[T, F, T, T]$


# Notation for Bits and Words

## Bits and Words

- $V w$  is the natural number represented in binary by  $w$ 
  - example:  $V [T; F; T; T] = 11$
  - $V : \text{bool list} \rightarrow \text{nat}$
  - $V w$  easily defined by primitive recursion on the length of  $w$
- Bit  $w i$  selects  $i$ th bit of  $w$

# Recursive Definition of an $n$ -bit Adder

## Primitive Recursive Definition

 

$$\vdash \text{Adder}([], [], cin, [], cout) = (cout = cin)$$

$$\vdash \text{Adder}((a_n :: a), (b_n :: b), cin, (s_n :: s), cout) =$$

$$\exists c. \text{Add}(a_n, b_n, c, s_n, cout) \wedge \text{Adder}(a, b, cin, s, c)$$

$$\text{Adder} : \text{bool list} \times \text{bool list} \times \text{bool} \times \text{bool list} \times \text{bool} \rightarrow \text{bool}$$

# Formulation of Correctness

- Specification

$$\vdash \text{AdderSpec } n (a, b, \text{cin}, s, \text{cout}) = ((2^n \times \text{cout}) + s = a + b + \text{cin})$$

- Correctness condition

$$\vdash \forall n a b \text{cin } s \text{cout}.$$

$$\text{Adder}(a, b, \text{cin}, s, \text{cout}) \Rightarrow$$

$$\text{AdderSpec}(\forall a, \forall b, \forall \text{cin}, \forall s, \forall \text{cout})$$


- Note the **data abstraction**

$\text{AdderSpec}(a, b, \text{cin}, s, \text{cout})$       numbers



$\text{Adder}(a, b, \text{cin}, s, \text{cout})$       words
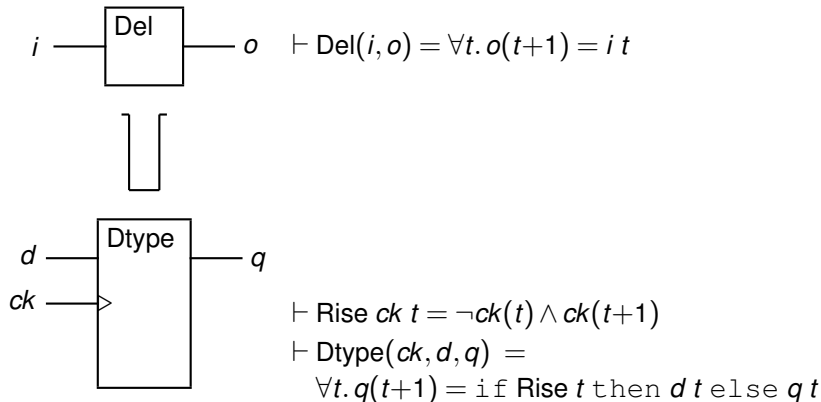
# Temporal Abstraction: example – abstracting to unit delay




- Notions of time involved:

- coarse grain of time – unit time = 1 clock cycle
- fine grain of time – unit time  $\approx$  1 gate delay



# Formulating Correctness

- A mapping between time-scales:

 

- Define the temporal abstraction functions:

$\vdash \text{Timeof } \mathcal{P} \ n = \text{the time } t_c \text{ such that } P \text{ is true for the } n\text{th time}$

$\vdash s \text{ when } P = s \circ (\text{Timeof } P)$

- Then correctness is stated by:

$\vdash \forall ck. \text{Inf}(\text{Rise } ck) \Rightarrow$

$\quad \forall d \ q. \text{Dtype}(ck, d, q) \Rightarrow$

$\quad \text{Del}(d \text{ when } (\text{Rise } ck), q \text{ when } (\text{Rise } ck))$

- Note the formal validity condition

$\vdash \text{Inf } P = \forall t. \exists t'. t' > t \wedge P \ t'$

# Outline

- 1 Introduction
- 2 Hardware Verification in HOL
  - General Approach
  - Composition
  - Verification
  - Full Adder Example
- 3 Summary

# Summary

## Summary

- Specifying behaviour:
  - predicates –  $\mathcal{S}[a, b, c, d]$
- Specifying/expressing structure:
  - composition –  $\mathcal{S}_1[a, x] \wedge \mathcal{S}_2[x, b]$
  - hiding –  $\exists x. \mathcal{S}_1[a, x] \wedge \mathcal{S}_2[x, b]$
- Formulating correctness:
  - $\vdash \forall v_1 \dots v_n. \mathcal{M}[v_1, \dots, v_n] = \mathcal{S}[v_1, \dots, v_n]$
  - $\vdash \forall v_1 \dots v_n. \mathcal{M}[v_1, \dots, v_n] \Rightarrow \mathcal{S}[v_1, \dots, v_n]$
  - $\vdash \forall v_1 \dots v_n. \mathcal{M}[v_1, \dots, v_n] \Rightarrow \mathcal{S}[\text{Abs } v_1, \dots, \text{Abs } v_n]$
- Abstraction:
  - data – mappings between data types
  - temporal – mappings between time scales

# Alternative Technique

## Embedding Semantics of HDLs in HOL

- lets you use the engineer-friendly HDL notation
- formally verify correctness properties
- metatheorems about HDL